

out of 29 points total
5 + 15 + 9

Xichen Jiang
ECE 476
HW 2
Fall 2012

Problem 1: Minimize real power line losses:

5 points

$$Q_{cap} = 4.0 \text{ MVAR}$$

2 points
per correct
answer,


Minimize MVA power flow into feeder:

$$Q_{cap} = 4.5 \text{ MVAR}$$

0.5 points per
labelling of units

Problem 2:

15 points

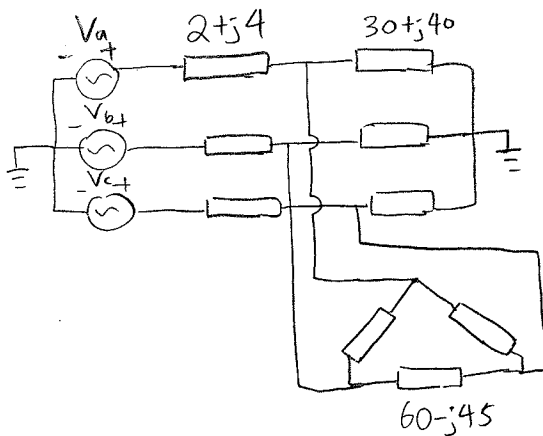


$$V_{ll} = 120\sqrt{3}$$

3 points,
one point
per
answer,

- Balanced load \Rightarrow Analyze each phase separately
First use Δ -Y transformation to turn delta load into
Y-load

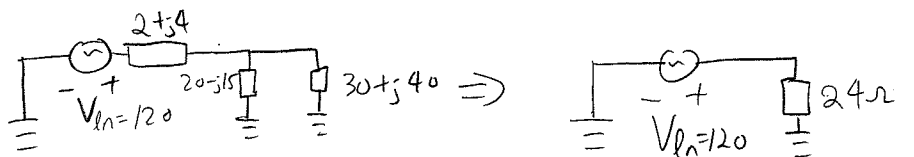- 0.5 points
for no
units

$$Z_{\Delta} = 60 - j45 \Rightarrow Z_Y = \frac{Z_{\Delta}}{3} = 20 - j15 \Omega$$



Assume phase 'a' has voltage angle 0° .

Problem 2:

1. Using KVL: $\bar{I}_\phi = \frac{120 \angle 0}{24} = \boxed{5A}$ or $5 \angle 0^\circ A$


$$S_\phi = V_\phi \bar{I}_\phi^* = 120 \cdot 5 = 600 \text{ VA}$$

$$S_{Tot} = 3 \cdot 600 = 1800 \text{ VA}$$

$$\boxed{P = 1800 \text{ W}}, \quad \boxed{Q = 0 \text{ VAR}}$$

2 points

2.

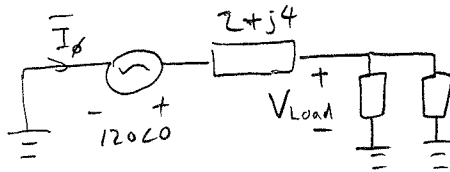

$$\bar{V}_{Load} = \bar{V}_\phi - \bar{I}_\phi (2 + j4)$$

$$\begin{aligned} \bar{V}_{Load} &= 120 \angle 0 - 5 \angle 0 \cdot (2 + j4) \\ &= 110 - j20 \\ &= 111.8 \angle -0.18 \end{aligned}$$

1 point for magnitude,
1 point for phase angle,
work must be shown
to earn credit


Assuming phase a line to neutral has phase 0° ,

\bar{V}_{ell} for phase a is:

$$\begin{aligned} \bar{V}_{ell} &= \sqrt{3} \bar{V}_{Load} e^{j(\pi/6)} \\ &= \boxed{193.6 \angle 0.34} \text{ V} \end{aligned}$$

$\uparrow 19.68^\circ$

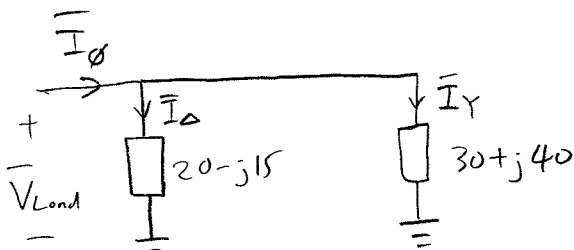3.
~~3 points~~
4 points,
two points
per
answer




$$\bar{I}_\Delta = \frac{\bar{V}_{Load}}{20 - j15} = \frac{111.8 \angle -0.18}{20 - j15} = 4 + j2 = 4.47 \angle 0.46$$

Since \bar{I}_Δ is current of equivalent Y load for the actual Δ load; we need the phase current through each load of Δ connection

Problem 2

3.

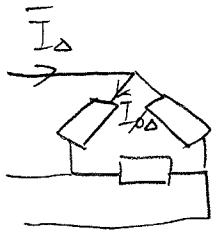

$$\vec{I}_{\phi\Delta} = \frac{\vec{I}_\Delta}{\sqrt{3}} \cdot e^{j(\pi/6)}$$

$$= \boxed{2.58 \angle 0.983 \text{ A}}$$

↑
56.57°

The angle will have diff. values depending on which phase is chosen and how the phase current is labeled. The magnitude must be 2.58.

$$\vec{I}_Y = \frac{\vec{V}_{Load}}{30 + j40} = \frac{111.8 \angle -0.18}{30 + j40} = 1 - j2 = \boxed{2.23 \angle -1.107 \text{ A}}$$

↳ -63.43°

6 points 4.

$$\Delta \text{ Load: } \vec{S}_\Delta = 3 \cdot (111.8 \angle -0.18)(4.47 \angle 0.46)^*$$

$$= 1200 - j900$$

$$\therefore \boxed{\vec{P}_\Delta = 1200 \text{ W}, \vec{Q}_\Delta = -900 \text{ VAR}}$$

$$Y \text{ Load: } \vec{S}_Y = 3 \cdot (111.8 \angle -0.18)(2.23 \angle -1.107)^*$$

$$= 450 + j600$$

$$\therefore \boxed{\vec{P}_Y = 450 \text{ W}, \vec{Q}_Y = 600 \text{ VAR}}$$

$$\text{Line: } \vec{S}_{Line} = 3 \cdot \frac{|\vec{V}_{drop}|^2}{\vec{Z}_{Line}^*} = 3 \cdot \frac{|120 \angle 0 - 111.8 \angle -0.18|^2}{2 - j4}$$

$$= 150 + j300$$

$$\therefore \boxed{\vec{P}_{Line} = 150 \text{ W}, \vec{Q}_{Line} = 300 \text{ VAR}}$$


Note: $\vec{I}\vec{I}^* = |\vec{I}|^2$ and $\vec{I} = \frac{\vec{V}}{\vec{Z}}$, $\vec{I}^* = \frac{\vec{V}^*}{\vec{Z}^*}$

Also, notice $\vec{S}_\Delta + \vec{S}_Y + \vec{S}_{Line} = 1800 \text{ W}$ (sanity check :))

Problem 3

9 points

Load:

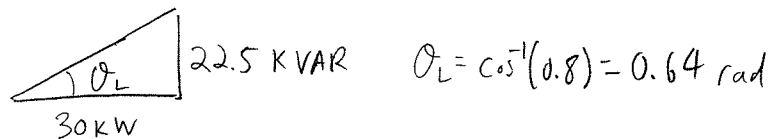

G1:



Doesn't matter if Load is Δ or Y since we're using per phase equivalent

$$460 \text{ V Line-Line} \Rightarrow \frac{460}{\sqrt{3}} \text{ V Line-Neutral}$$

↑ Let this be 0° phase reference.
Of course we can also make life hard by letting this have a 30° phase shift.

$$\begin{aligned} \text{Current of G1 Line: } \bar{I}_{G1} &= \left(\frac{\bar{S}_{G1}}{3\bar{V}_{G1}} \right)^* = \frac{15 - j11.25}{3 \left(\frac{460}{\sqrt{3}} \right)} \leftarrow \text{in kVA} \\ & \text{per phase} \nearrow \\ &= 18.83 - j14.11 \text{ A} \\ &= \boxed{23.53 \angle -0.643 \text{ A}} \\ & \quad \hookrightarrow -36.84^\circ \end{aligned}$$

3 points 1. Voltage at Load terminals:

$$\text{Using KVL: } \frac{460}{\sqrt{3}} \angle 0 = \bar{I}_{G1} \cdot (1.4 + j1.6) + \bar{V}_{\text{Load}}$$

$$\begin{aligned} \bar{V}_{\text{Load}} &= 216.6 - j10.37 \text{ V} \\ &= \boxed{216.89 \angle -0.047 \text{ V}} \quad \text{Line-Neutral} \\ & \quad \hookrightarrow -2.74^\circ \end{aligned}$$

$$\text{or } 375.6 \angle 27.26^\circ \text{ V Line-Line}$$

Problem 3

3 points 2.

$$\bar{I}_{\text{Load}} = \left(\frac{\bar{S}_{\text{Load}}/3}{\bar{V}_{\text{Load}}} \right)^* = \frac{10 - j7.5}{216.6 + j10.37} = 44.41 - j36.75 \text{ A}$$

$$\begin{aligned} \bar{I}_{G2} &= \bar{I}_{\text{Load}} - \bar{I}_{b1} = 44.41 - j36.75 - (18.83 - j14.11) \\ &= 25.58 - j22.64 \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{V}_{G2} &= \bar{V}_{\text{Load}} + \bar{I}_{G2}(0.8 + j1) \\ &= 216.6 - j10.37 + (25.58 - j22.64)(0.8 + j1) \\ &= 259.7 - j2.9 \text{ V} \\ &= \boxed{259.7 \angle -0.011 \text{ V}} \\ &\quad \hookrightarrow -0.64^\circ \end{aligned}$$

3 points 3.

$$\begin{aligned} \bar{S}_{G2} &= 3 \cdot \bar{V}_{G2} \bar{I}_{G2}^* \\ &= 3(259.7 \angle -0.011)(25.58 + j22.64) \\ &= \boxed{20.13 + j17.4 \text{ kVA}} \end{aligned}$$

↑ ↑
P Q