


$$8 + 15 + 6 + 3 = \boxed{32 \text{ points}}$$

Xichen Jiang
HW 6
ECE 476

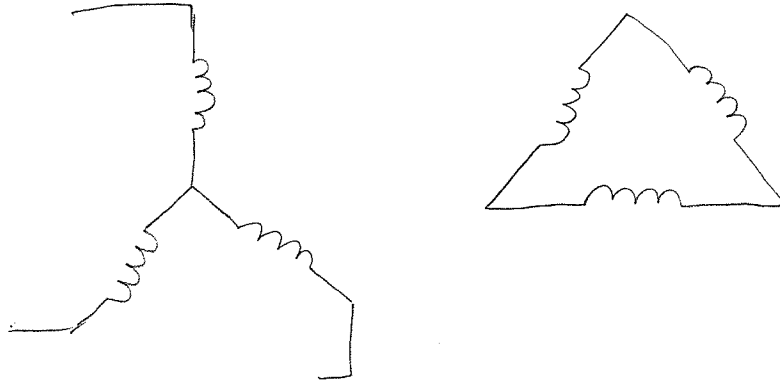Problem 1

8 points

Draw out the Y- Δ circuits for better visualization.



Each winding on Y-side must handle line-neutral voltage while on Δ -side, line-line voltage. Power rating will be same on both sides.

a) Each Transformer ratings:

$$\text{Power: } \frac{2.1 \text{ MVA}}{3} = \boxed{0.7 \text{ MVA}} \text{ both sides}$$

2 points

$$\text{Voltage: } \frac{13.8}{\sqrt{3}} : 2.3 = \boxed{7.96 \text{ kV (Wye)} : 2.3 \text{ kV (Delta)}}$$

$$\text{Current: } \frac{0.7}{7.96} = \boxed{87.94 \text{ A (Wye)}}$$

$$\frac{0.7}{2.3} = \boxed{304.3 \text{ A (Delta)}}$$

Problem 1

b) Power: 0.7 MVA

Voltage: $13.8 : \frac{2.3}{\sqrt{3}} = 13.8 \text{ kV (Delta)} : 1.33 \text{ kV (Wye)}$

2 points Current: $\frac{0.7}{13.8} = 50.7 \text{ A (Delta)}$

526.3 A (Wye)

c) Power: 0.7 MVA

2 points Voltage: $7.96 \text{ kV} : 1.33 \text{ kV}$

Current: $87.94 \text{ A on High Side}$

$526.3 \text{ A on Low Side}$

d) Power: 0.7 MVA

2 points Voltage: $13.8 \text{ kV} : 2.3 \text{ kV}$


Current: 50.7 A High Side

304.3 A Low Side

Problem 2

15 points

↳ 5+4+4+2

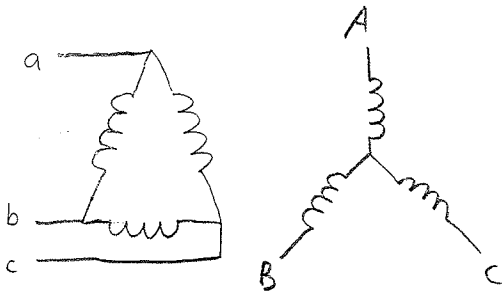

$X_L = 0.11 \text{ p.u.}$

Problem 2

a) Some clarification first... (this was not added in original problem because all power engineers speak like this in industry \Rightarrow students should get used to it).

i) 230 kV \Rightarrow line-line voltage (standard voltage), positive seq. assumed

ii) $S_{Base} = 100$ MVA for entire system

Each transformer has its own power base equal to its rating. In this case, it's 330 MVA, which is independent of $S_{Base} = 100$ MVA. This way, X_l can be stated in p.u. independent of the system.

iii) $X_l = 0.11$ p.u. if for 1ϕ .

Now, supply system load of 240 MVA at 0.9 pf lag

$$\Rightarrow |\bar{I}_A| = |\bar{I}_B| = |\bar{I}_C| = \frac{S_{load}}{V_{line-neutral}} = \frac{240/\sqrt{3} \text{ MVA}}{230/\sqrt{3} \text{ kV}} = 602.45 \text{ A}$$

\leftarrow think per phase equivalent ($3\phi Y$ to 1ϕ)
 \therefore line-neutral

$$\bar{V}_A = 1.0 \angle 0^\circ \text{ p.u.}, \quad \theta = \cos^{-1}(0.9) = 25.8^\circ \Rightarrow \theta_i = -25.8^\circ \text{ (lag)}$$

$$\therefore \bar{I}_A = 602.45 \angle -25.8^\circ \text{ A}$$

$$\bar{I}_B = 602.45 \angle -145.8^\circ \text{ A}$$

$$\bar{I}_C = 602.45 \angle 94.2^\circ \text{ A}$$

To find p.u., we need $I_{Base, 1\phi} = \frac{S_{B.u., 1\phi}}{V_{Base, l-n}} = \frac{100 \text{ MVA}}{\frac{230}{\sqrt{3}} \text{ kV}} = 251.02 \text{ A}$

\therefore In per unit,

$$\frac{\bar{I}_A}{I_{Base, 1\phi}} = \bar{I}_{A,p.u.} = \frac{602.45}{251.02} \angle -25.8^\circ = \boxed{2.4 \angle -25.8^\circ}$$

~~$$\bar{I}_B = 602.45 \angle -145.8^\circ \text{ A}$$~~

$$\bar{I}_{B,p.u.} = \boxed{2.4 \angle -145.8^\circ}$$


$$\bar{I}_{C,p.u.} = \boxed{2.4 \angle 94.2^\circ}$$

5 points

\hookrightarrow 2 for work, 3 for answers

Problem 2

b)

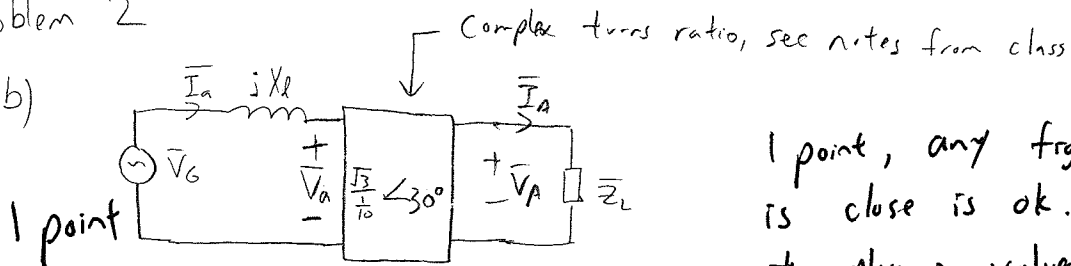

1 point

1 point, any figure that is close is ok. No need to plug in values.

$$\bar{I}_a = \frac{\bar{I}_A}{\frac{1}{10} \angle 30^\circ} \quad \text{but in p.u., magnitudes of current do not change, only } \bar{I}_{Base} \text{ changes}$$

∴ just account for the phase shift.

$$\bar{I}_{a,p.u.} = \bar{I}_{A,p.u.} \cdot e^{-j(\frac{\pi}{6})} = \boxed{2.4 \angle -55.8^\circ}$$

3 points $\bar{I}_{b,p.u.} = \boxed{2.4 \angle -175.8^\circ}$

$$\bar{I}_{c,p.u.} = \boxed{2.4 \angle 64.2^\circ}$$

c) First, we need X_L . Although it is given p.u., it's not the system p.u. To see this, find X_L in Ω 's first.

2 points for work,

2 points for answer,

each answer gets 1 point

$$X_{L,\Omega} = 0.11 \times Z_{Base, Transformer} = 0.11 \times 1.603 = 0.176 \Omega$$

For Δ side (Low side), $Z_{Base, Transformer} = \frac{V_{Base}^2}{S_{Base}} = \frac{(\frac{23kV}{\sqrt{3}})^2}{\frac{330}{3} MVA} = 1.603 \Omega //$

To find $X_{L,p.u}$ in system, use $Z_{Base, system} = \frac{(\frac{23kV}{\sqrt{3}})^2}{\frac{100}{3} MVA} = 5.29 \Omega //$

$$\therefore X_{L,p.u.} = \frac{0.176}{5.29} = \underline{\underline{0.0333 \text{ p.u.}}}$$

Alternatively, $X_{L,p.u.} = 0.11 (\frac{100}{330}) = \frac{1}{30}$, which matches above.

KVL: $\bar{V}_G = \bar{I}_a \cdot jX_{L,p.u.} + \bar{V}_a$

$$= 2.4 \angle -55.8^\circ (j0.0333) + 1 \angle -30^\circ$$

$$= 0.932 - j0.455 \text{ p.u.} //$$

$$= 1.037 \angle -26.02^\circ \text{ p.u.}$$

↳ see notes, $\bar{V}_a = \bar{V}_A \angle -30^\circ$

Problem 2

$$\begin{aligned} \text{c) } \bar{V}_G &= 23 \text{ kV} \cdot 1.037 \angle -26.02^\circ \\ &= 23.85 \angle -26.02^\circ \text{ kV for phase A} \end{aligned}$$

$$\Rightarrow \text{Magnitude} = \boxed{23.85 \text{ kV}}$$

$$\begin{aligned} \bar{S}_G &= \bar{V}_G \bar{I}_a^* = (1.037 \angle -26.02^\circ) (2.4 \angle 55.8^\circ) \\ &= 2.48 \angle 29.78^\circ \text{ p.u.} \end{aligned}$$

$$\Rightarrow P_{G, \text{p.u.}} = 2.15$$

$$P_{G, 3\phi} = 2.15 \times 100 = \boxed{215 \text{ MW } 3\phi}$$

Short-cut: No loss ($R=0$) \Rightarrow all power supplied goes to load

$$\therefore P_{G, 3\phi} = 240 \text{ MVA} \cdot \underset{\text{PF}}{0.9} = 216 \text{ MW} //$$

2 points
d)

Check. $|\bar{V}_G|$ should stay same, $P_{G, 3\phi}$ stay same (duh, no loss in system)

1 point for showing effort (right or wrong), i.e., show work

1 point for correct conclusion

Problem 3


6 points a)

High voltage windings are Wye

Low voltage Wye \Rightarrow No phase shift.

Let $S_{Base} = 10 \text{ MVA}$, $V_{Base_{High}} = \frac{115 \text{ kV}}{\sqrt{3}} = 66.4 \text{ kV}$, $V_{Base_{Low}} = 12.5 \text{ kV}$
 \hookrightarrow l-n

Equivalent Circuit:

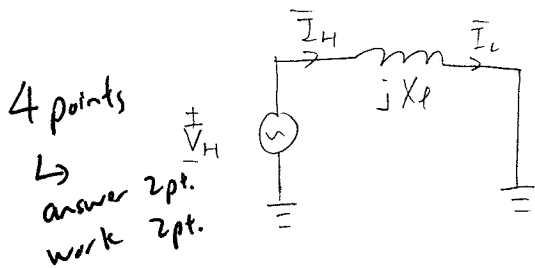

Everything is Line-Neutral

$$I_{Base_{High}} = \frac{S_{Base}}{V_{Base_{High}}} = \frac{10 \text{ MVA}}{66.4 \text{ kV}} = 150.6 \text{ A}$$

$$I_{Base_{Low}} = \frac{S_{Base}}{V_{Base_{Low}}} = \frac{10 \text{ MVA}}{12.5 \text{ kV}} = 800 \text{ A}$$

$$\bar{I}_H = \bar{I}_L = \frac{\bar{V}_H}{jX_L} = \frac{1 \angle 0^\circ}{j0.1} = 10 \angle -90^\circ \text{ p.u.}$$

$$\therefore |\bar{I}_H| = 10 \cdot 150.6 = \boxed{1506 \text{ A}}$$

$$|\bar{I}_L| = 10 \cdot 800 = \boxed{8000 \text{ A}}$$

b) $I_{Base_{High}}$ stays same. $I_{Base_{Low}}$ changes since $V_{Base_{Low}}$ is changed

2 points



each of these can handle 12.5 kV \Rightarrow Δ to for phase equivalent, we need line-N

$$I_{Base_{Low}} = \frac{S_{Base}}{V_{Base_{Low}}} = \frac{10 \text{ MVA}}{\frac{12.5 \text{ kV}}{\sqrt{3}}} = 138.5 \text{ A}$$

$$|\bar{I}_H| = \boxed{1506 \text{ A}}$$

$$|\bar{I}_L| = 10 \cdot 138.5 = \boxed{1385 \text{ kA}}$$

Problem 4

3 points

Phase Shift Angle	Real Power Loss (MW)
-10°	24.91
-9°	23.37
-8°	21.99
-7°	20.77
-6°	19.70
-5°	18.79
-4°	18.04
-3°	17.44
-2°	17.01
-1°	16.73
0°	16.60
1°	16.64
2°	16.83
3°	17.19
4°	17.69
5°	18.36
6°	19.18
7°	20.16
8°	21.30
9°	22.59
10°	24.04

0° minimizes real power loss

2 points
1 point for table OR if sketch is labeled with correct axis values

1 point for answer 0°

Sketch

1 point for sketch. If sketch is labelled with correct values on axes, table above is not needed

