

$$5+5+7+3 = \boxed{20 \text{ points}}$$

Xichen Jiang
ECE 476
HW 7

Problem 1

$\boxed{5 \text{ points}}$

5 buses $\Rightarrow Y_{bus}$ is 5×5 matrix

row 3 \Rightarrow Need admittances connected to bus 3

$Y(3,3) =$ Sum of admittances connected to bus 3

$$= \frac{1}{R_{34} + jX_{34}}$$

$$= \frac{1}{0.00075 + j0.01}$$

$$= 7.46 - j99.4 \text{ p.u.}$$

$Y(3,1) = Y(3,2) = Y(3,5) = 0$ (No connection between these buses)


$$Y(3,4) = -Y(3,3) = -7.46 + j99.4 \text{ p.u.}$$

$$\therefore \boxed{\bar{Y}(3,*) = [0 \quad 0 \quad 7.46 - j99.4 \quad -7.46 + j99.4 \quad 0]}$$

1 point per answer

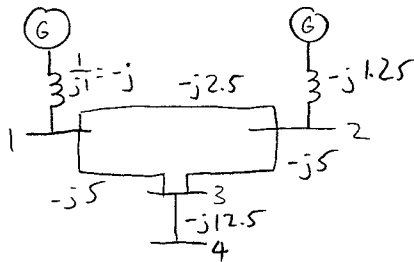Problem 2

$\boxed{5 \text{ points}}$
 $Y = \frac{1}{Z}$




$$Y_{bus} = \begin{bmatrix} -j8.5 & j2.5 & j5 & 0 \\ j2.5 & -j8.75 & j5 & 0 \\ j5 & j5 & -j22.5 & j12.5 \\ 0 & 0 & j12.5 & -j12.5 \end{bmatrix}$$

-1 for each wrong answer in matrix

Problem 3

7 points

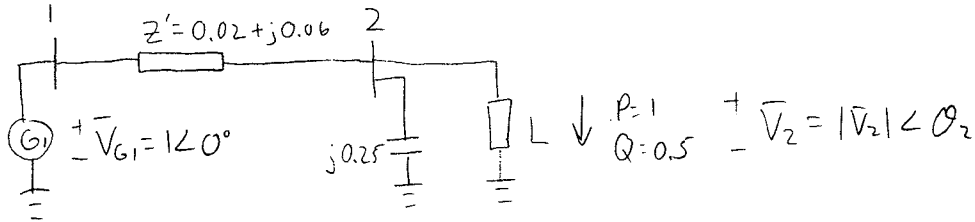

1 point a) See Figure above

b) Two buses $\Rightarrow Y_{bus}$ is 2×2 , $Y' = \frac{1}{Z'} = 5 - j15$

2 points

$$Y_{bus} = \begin{bmatrix} 5 - j15 & -5 + j15 \\ -5 + j15 & 5 - j14.75 \end{bmatrix}$$

c) Bus 1:

4 points

$$P_1 = |\bar{V}_{G1}|^2 [5 \cos(\theta_1 - \theta_1) - 15 \sin(\theta_1 - \theta_1)] + |\bar{V}_{G1}| |\bar{V}_2| [-5 \cos(\theta_1 - \theta_2) + 15 \sin(\theta_1 - \theta_2)]$$

$$P_1 = 5 + |\bar{V}_2| [-5 \cos(\theta_2) - 15 \sin(\theta_2)] ; \text{ since } \theta_1 = 0, |\bar{V}_{G1}| = 1$$

$$Q_1 = |\bar{V}_{G1}|^2 [5 \sin(\theta_1 - \theta_1) + 15 \cos(\theta_1 - \theta_1)] + |\bar{V}_{G1}| |\bar{V}_2| [-5 \sin(\theta_1 - \theta_2) - 15 \cos(\theta_1 - \theta_2)]$$

$$Q_1 = 15 + |\bar{V}_2| [5 \sin(\theta_2) - 15 \cos(\theta_2)]$$

Bus 2:

$$P_2 = |\bar{V}_2|^2 [5 \cos(\theta_2 - \theta_2) - 14.75 \sin(\theta_2 - \theta_2)] + |\bar{V}_2| |\bar{V}_{G1}| [-5 \cos(\theta_2 - \theta_1) + 15 \sin(\theta_2 - \theta_1)]$$

$$P_2 = 5 |\bar{V}_2|^2 + |\bar{V}_2| [-5 \cos(\theta_2) + 15 \sin(\theta_2)] = -1$$

← given load real power

$$Q_2 = |\bar{V}_2|^2 [5 \sin(\theta_2 - \theta_2) + 14.75 \cos(\theta_2 - \theta_2)] + |\bar{V}_{G1}| |\bar{V}_2| [-5 \sin(\theta_2 - \theta_1) - 15 \cos(\theta_2 - \theta_1)]$$

$$Q_2 = 14.75 |\bar{V}_2|^2 + |\bar{V}_2| [-5 \sin(\theta_2) - 15 \cos(\theta_2)] = -0.5$$

Note: P_2 is '-1' because the load draws 1 p.u. of real power \Rightarrow injects -1 p.u. into bus 2.

Problem 4

3 points

Effects on \bar{V}_2 : with the new line, $|\bar{V}_2|$ increase

Line Loadings: All other lines have % loading that decreased except for line 4-5

Real Power Losses: There's less real power losses (decreased)

For details, see table below.

	Before Addition of Line	After Addition of Line
Bus Voltage V_2 [p.u.]	0.834	0.953
Total real power losses [MW]	34.8	18.3
Branch b/w bus 1-5 (% loading)	68.5	63.1
Branch b/w bus 2-4 (% loading)	27.3	17.5
Branch b/w bus 2-5 (% loading)	49.0	25.4 (both lines)
Branch b/w bus 3-4 (% loading)	53.1	45.7
Branch b/w bus 4-5 (% loading)	18.8	22.1