

In The Name of Almighty

Lec. 8:
Subranging/Two-step ADCs

Lecturer: Hooman Farkhani

Department of Electrical Engineering


Islamic Azad University of Najafabad

Feb. 2016.

Email: H_farkhani@yahoo.com

General Concept of Multi-Step Conversion

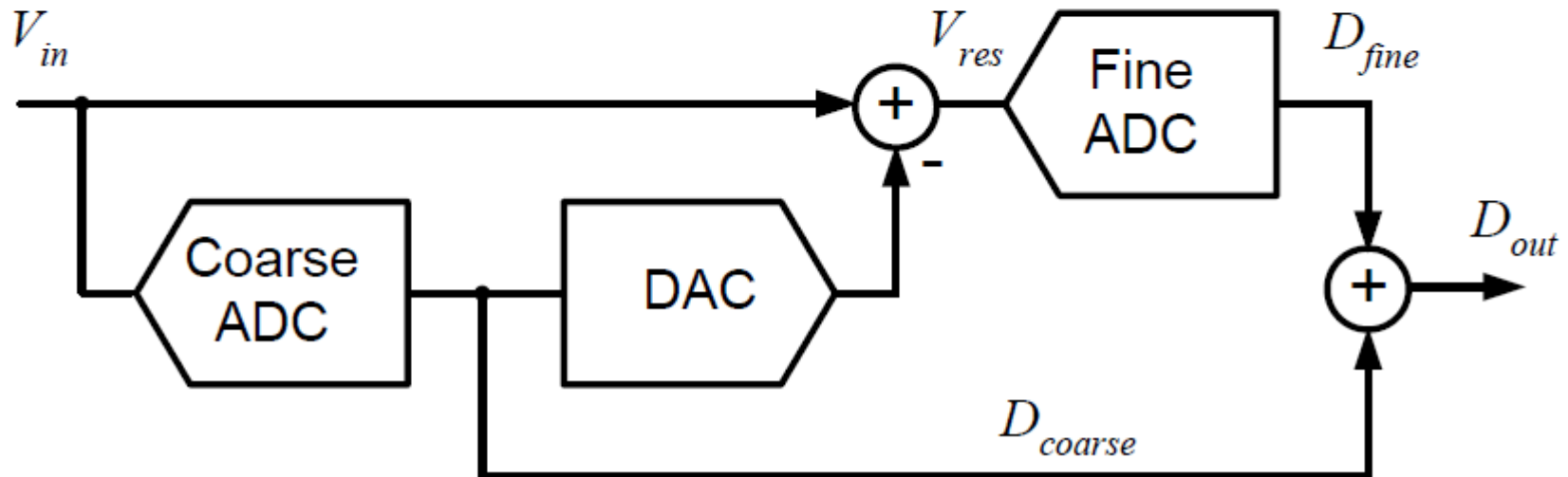- General idea (two-step example)
 1. Perform a "coarse" quantization of the input
 2. Compute residuum (error) of step 1 conversion using a DAC and subtractor
 3. Digitize computed residuum using a second "fine" quantizer and digitally add to output



Subranging & Two-step Converters

- When the **resolution is higher than 8-bit** then instead of **full-flash ADC**, it can be more convenient to use a sub-ranging or a two-step algorithm for a better speed-accuracy trade-off.
- The **sub-ranging or the two-step implementation** require **two (or three) clock periods** to complete the conversion but they use a smaller number of comparators thus **benefitting silicon area, power consumption and parasitic capacitance** loading on the *S&H*.
- The architecture uses a sample-and-hold at the input to drive an *M-bit* flash-converter which estimates the ***MSBs* (coarse conversion)**. The *DAC* then converts the *M-bits* back to an analog signal which is subtracted from the held input to give the coarse quantization error (also called the residue). Next, the residue is converted into digital by a second ***N-bits* flash** which yields the ***LSB* (fine conversion)**. The digital logic combines coarse and fine results to obtain the $n=(M+N)$ -bit output.
- **Sub-ranging**: without gain (No amplification of residue)
- **Two-step**: With amplifying the residue.

Sub-ranging/ Two-step


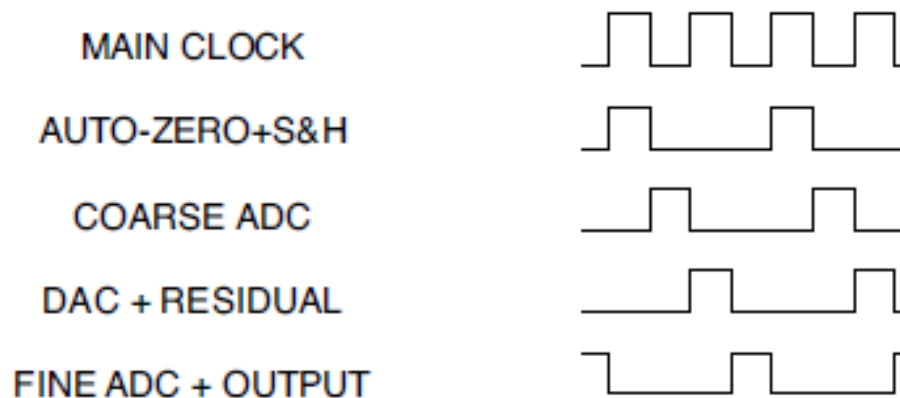
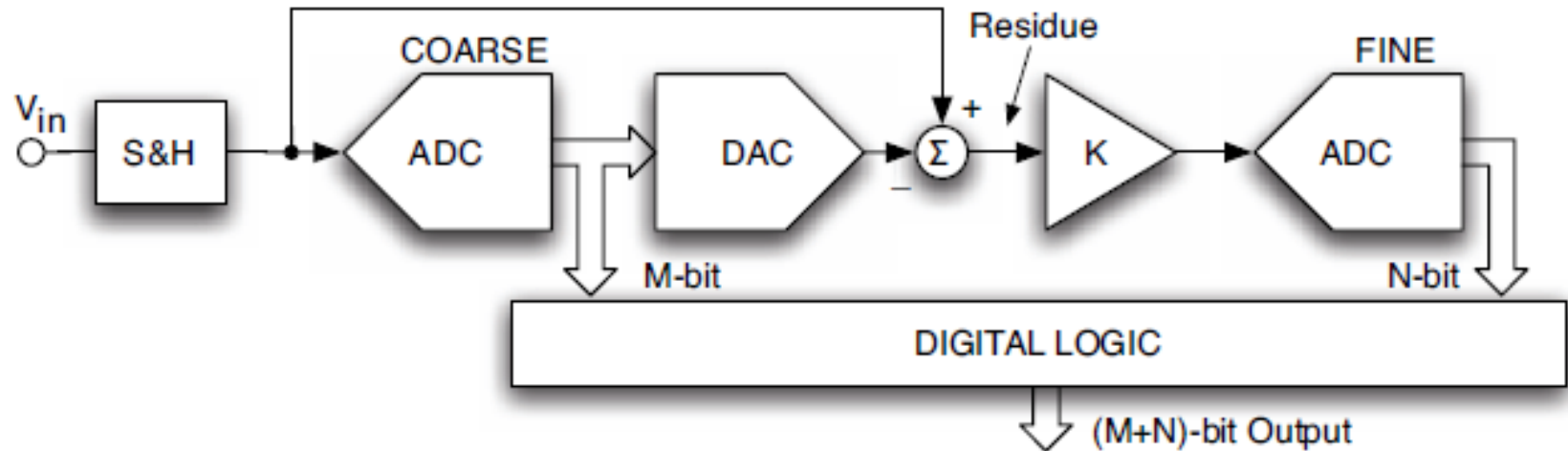



Figure 4.10. Block diagram of sub-ranging ($K=1$) and two-step architectures ($K>1$).

4-Bit Flash Vs. 4-Bit Two-Step ADC

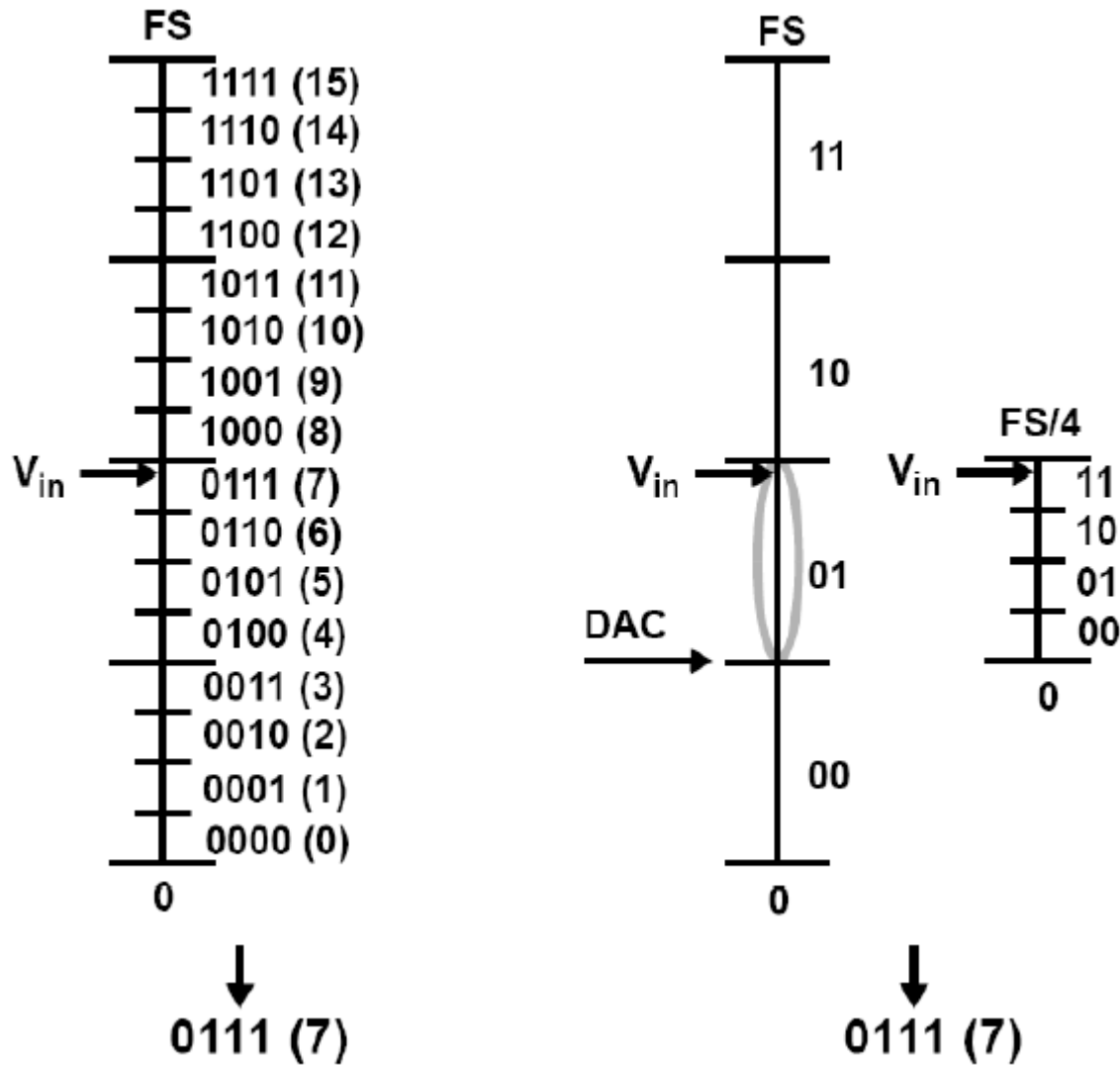

Sub-ranging ADC

➤ Principal of Operation:

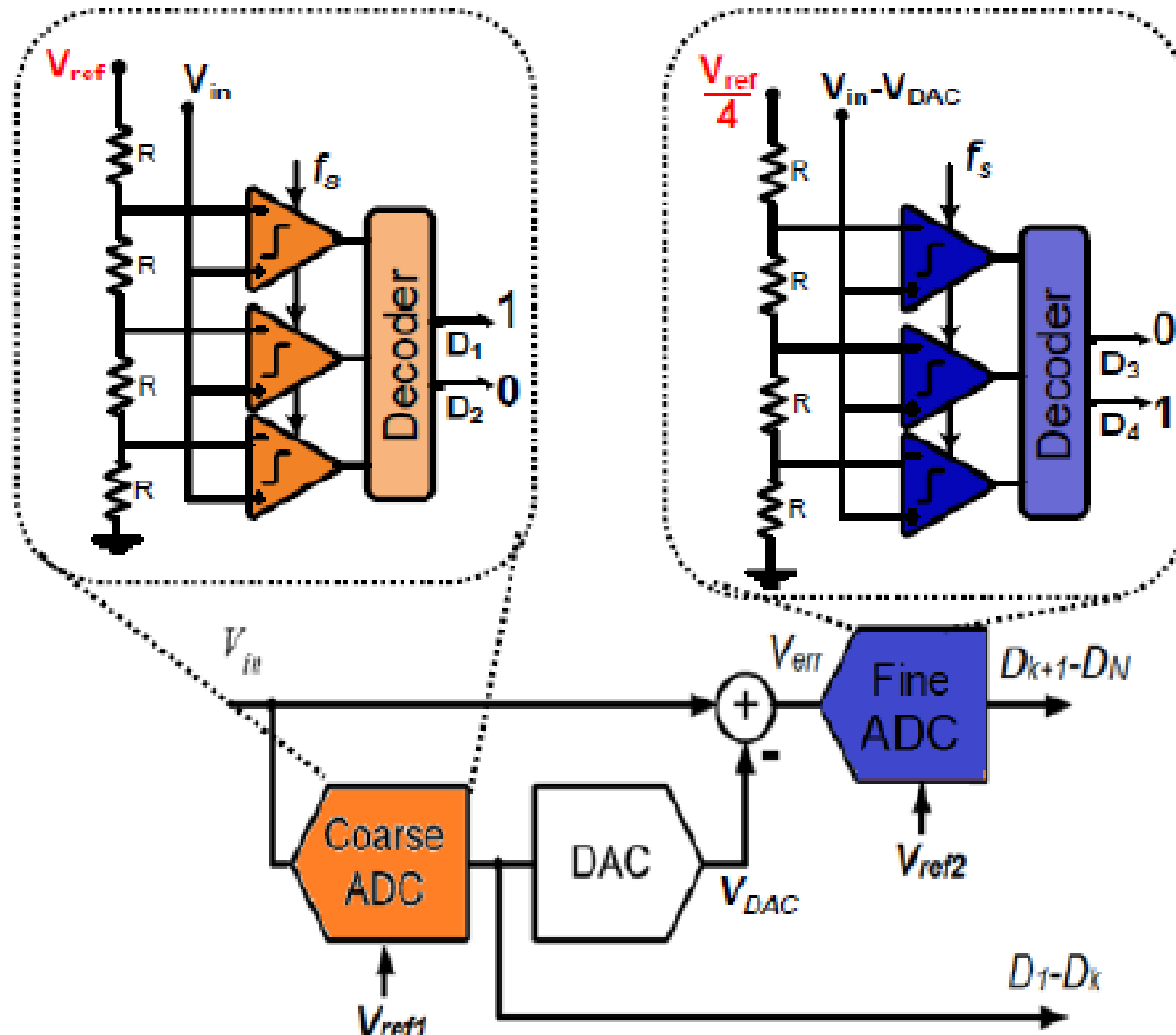

Pros/ Cons

■ Pros:

- ✓ The Number of comparators is significantly reduced in compare with the full-flash ADC
 - e.g. : for **8-bit** ($M=N=4$), $2*(2^4-1)=30$ **comparators** are needed while for full-flash ($2^8-1=255$) comparators are needed.
- ✓ The spared **area and power** are much more than what is required to design the DAC and residue generator; moreover, the *S&H* is only loaded by 2^M comparators.

■ Cons:

- ❖ Reduced conversion-rate as it is necessary to use two or three clock periods to complete the conversion. (But S/H is faster in sub-ranging due to the reduced parasitic input capacitance).

Delay of the Sub-ranging/Two-step ADC and possible Solution

- Conversion time :


$$T_{\text{conversion}} = T_{\text{course-ADC}} + T_{\text{DAC}} + T_{\text{subtractor}} + T_{\text{fine_ADC}}$$

- Solution:

Introduce a **sample and hold** operation after subtraction


→ During one clock cycle coarse & fine ADCs operate concurrently:

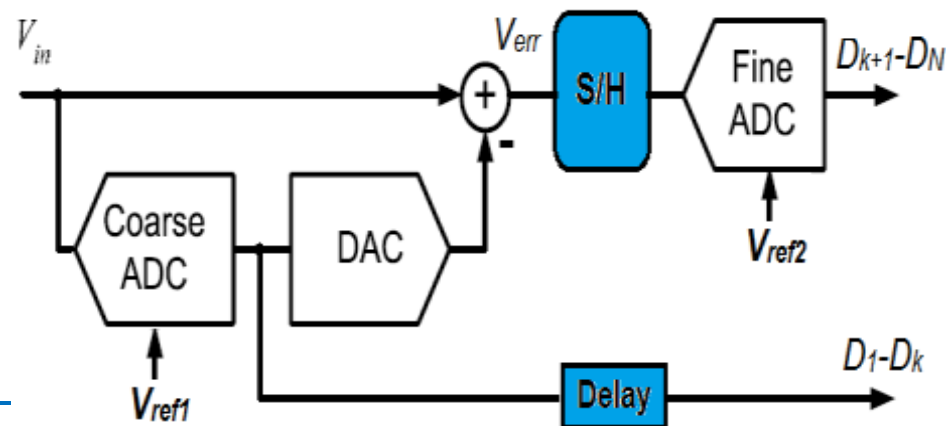First stage samples/converts/generates residue of input signal sample # i While 2nd stage samples/converts residue associated with sample # $i-1$




The advantage of using Gain stage (A) in Two-step over sub_ranging

- Without amplifying the residue (without gain stage):
 - ❖ The Fine ADC has to have precision in **the order of overall ADC 1/2LSB**
 - E.g. 8 bit converter with 4-bit /4-bit partition; fine 4-bit decision levels must have “8-bit precision”
- **Solution:** Introduce Gain after Subtraction:
 - Accuracy needed for fine ADC relaxed by introducing inter-stage gain
 - All stages use a single Vref
 - Advantageous for noise, matching and power dissipation

 


Quantization+Amplification

 


Two-Step principle of operation

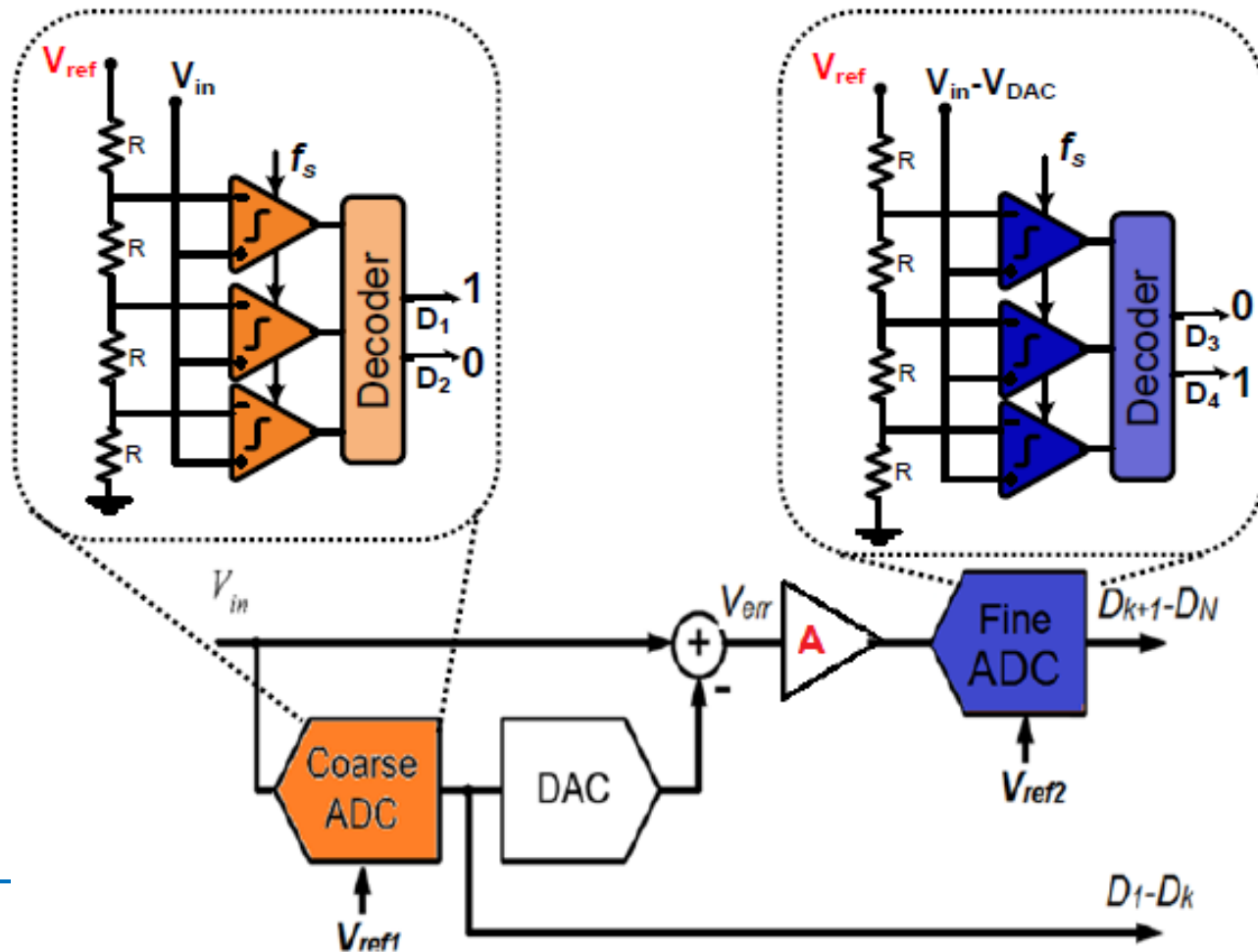
- Both coarse and fine ADC use V_{ref} . (in contrast to sub-Ranging i.e., V_{ref} for coarse and $V_{ref}/4$ for fine ADC-see slide 6)




How Much gain?

 


- For $M=1$ bit,

 

- For $M=2$ bits

 

- For $M=3$ bits

 

Accuracy Requirement


- Since the residue, determined by coarse *ADC*, *DAC* and gain factor *K*, is

$$V_{res}(V_{in}) = K [V_{in} - V_{DAC}(i)]$$


for : $V_{Coarse}(i - 1) \leq V_{in} < V_{Coarse}(i)$;

- ideal *ADC* and *DAC* give rise to a residue that is a perfect sawtoothed non linear function of the input with amplitude confined between 0 and $VFS \cdot K/2^M$.
- However, limitations of the *ADC* and *DAC* cause errors on the break points and amplitude of the sawtooth.


Two-Step ADC – Ideal

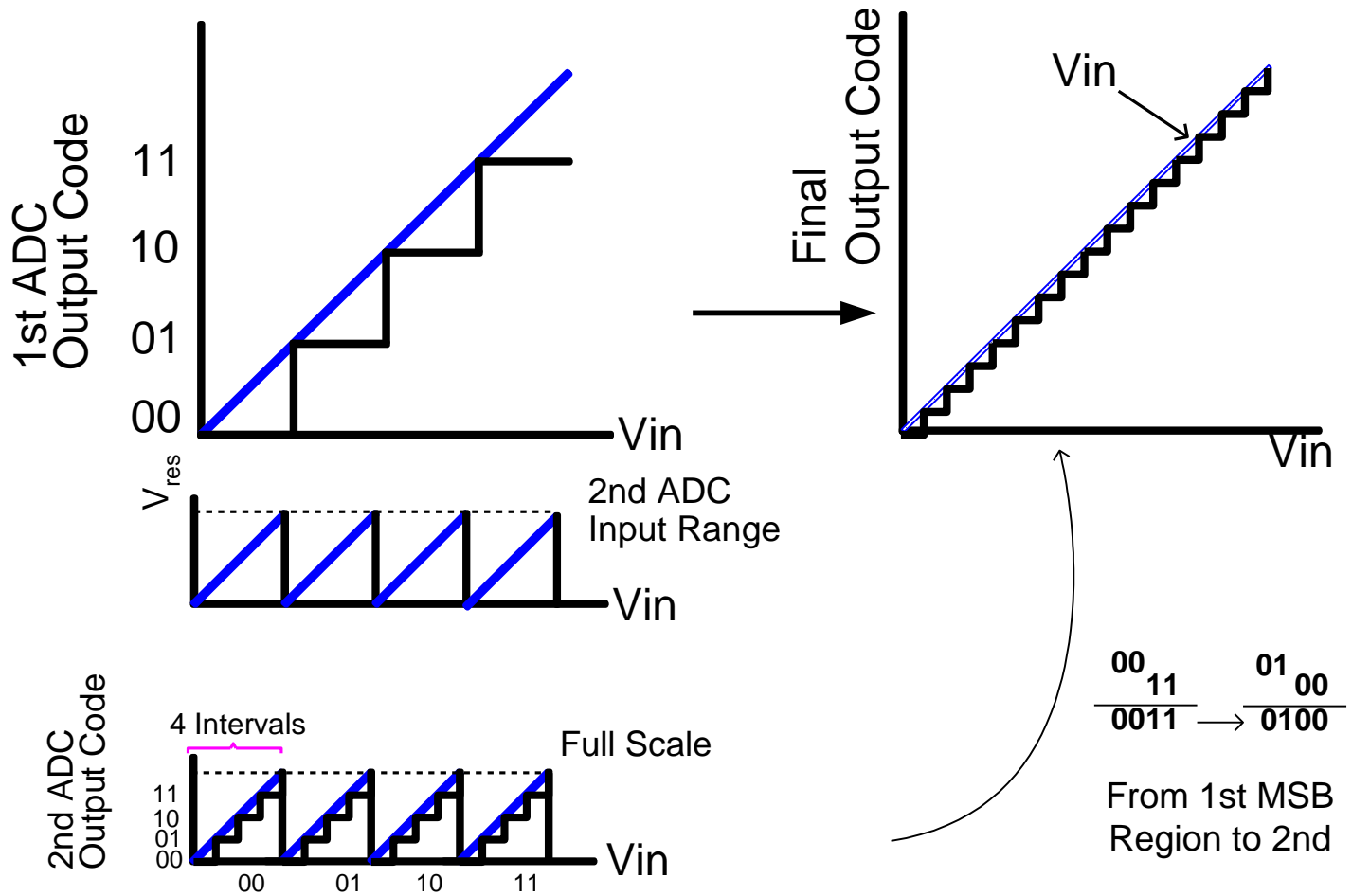

Two-Step ADC – DNL Error

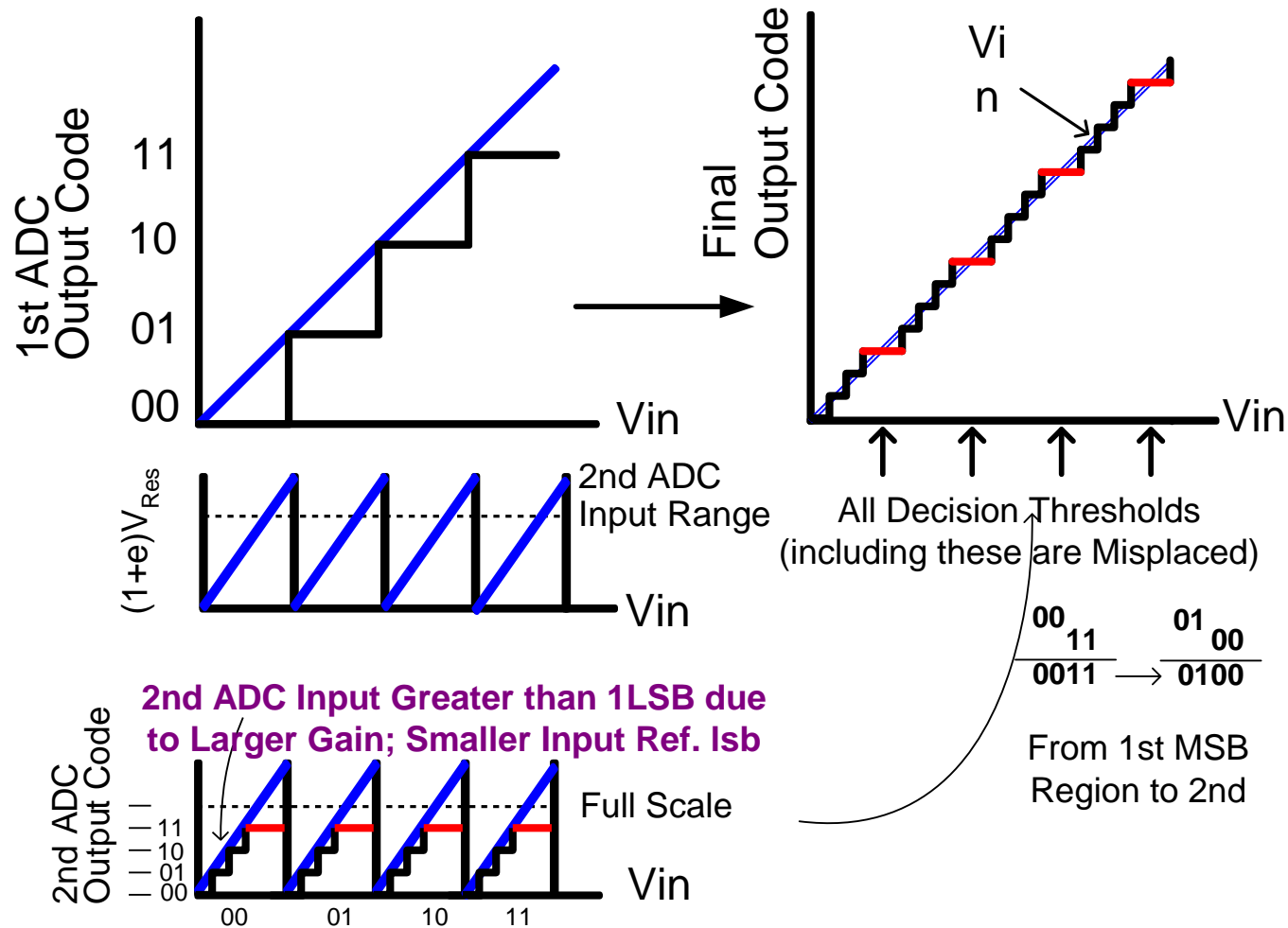

Two-Step ADC – Missing Codes

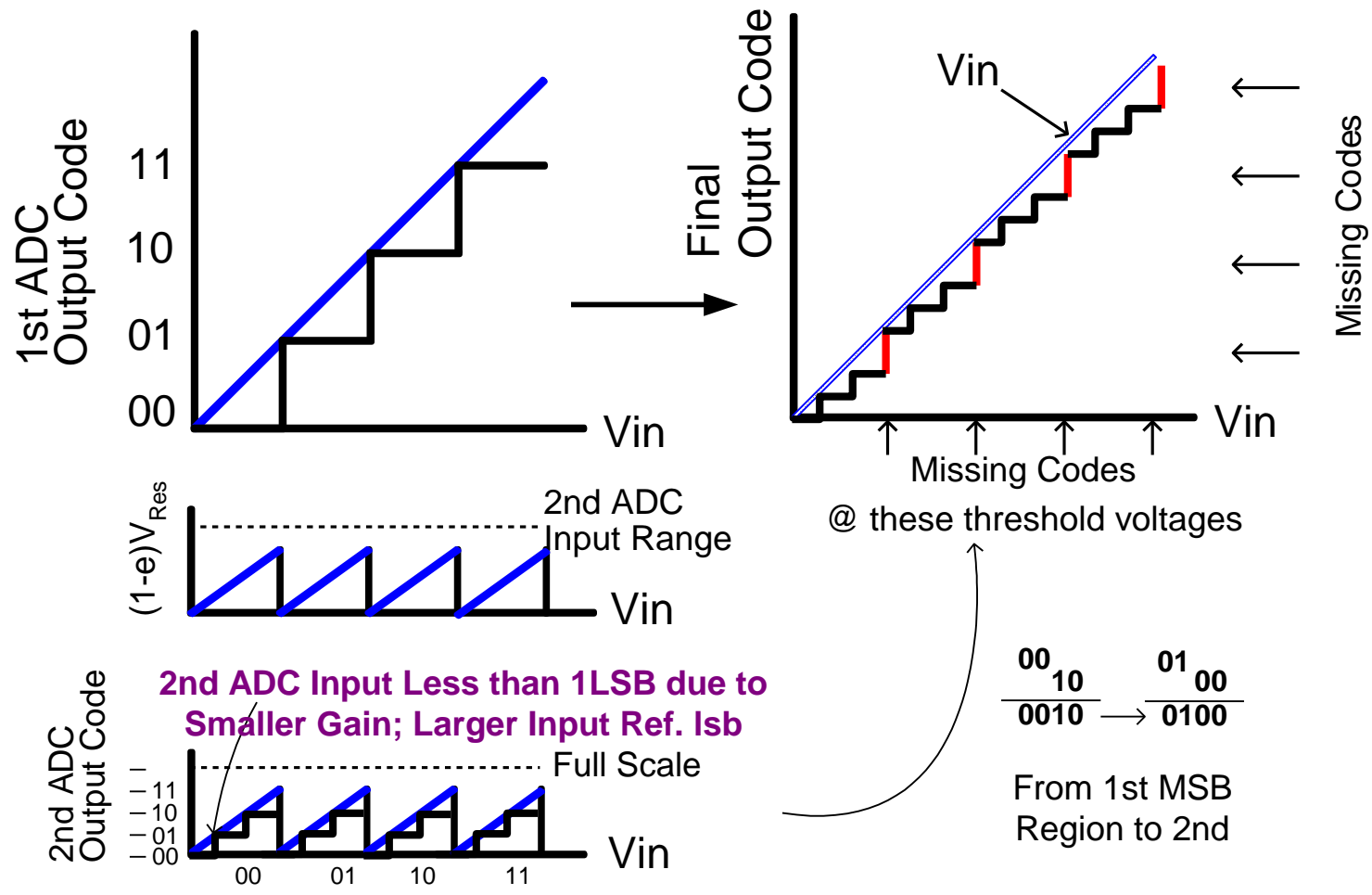

Real ADC with IDEAL DAC

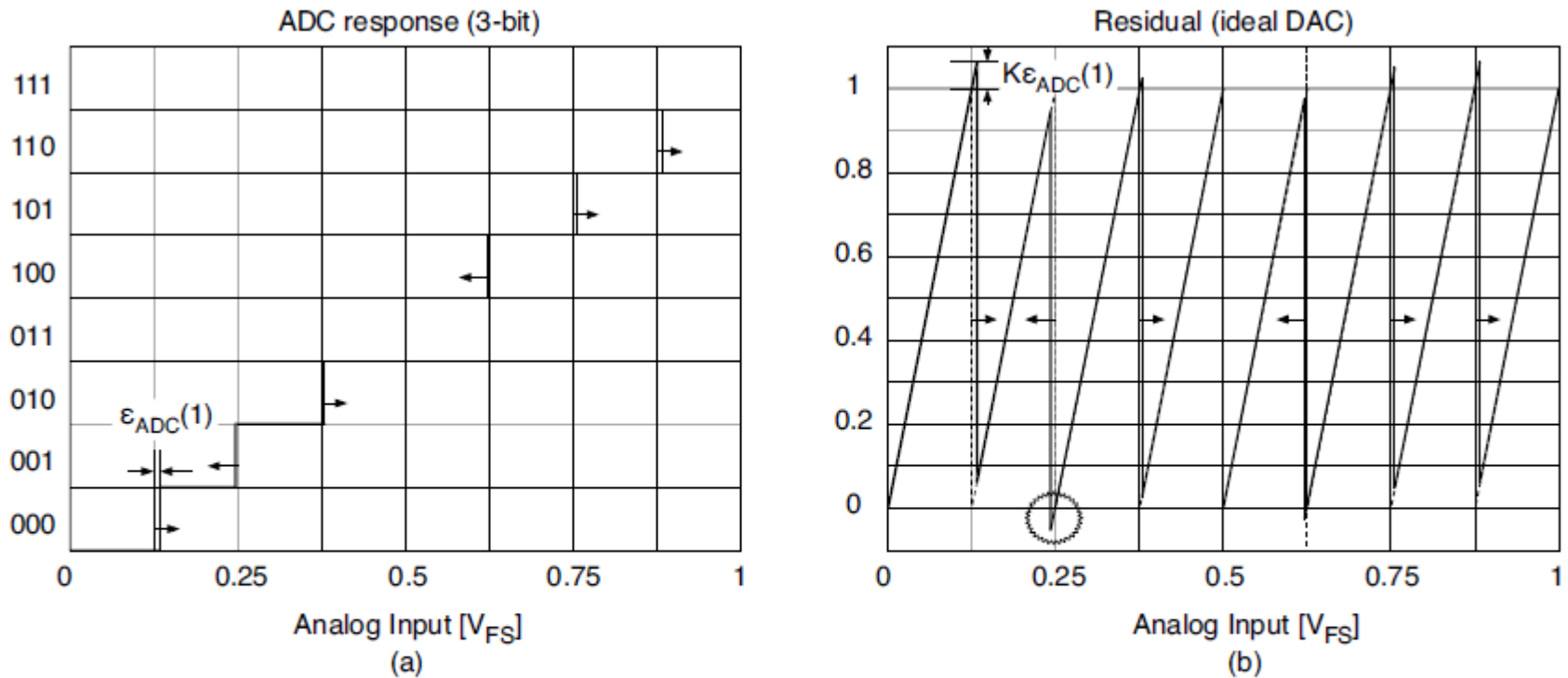


Figure 4.11. (a) Response of a real coarse ADC (3-bit). (b) Residue with ideal DAC.

IDEAL ADC with REAL DAC


 


Figure 4.12. (a) Response of a real DAC (3-bit). (b) Residue with real DAC and ideal ADC.


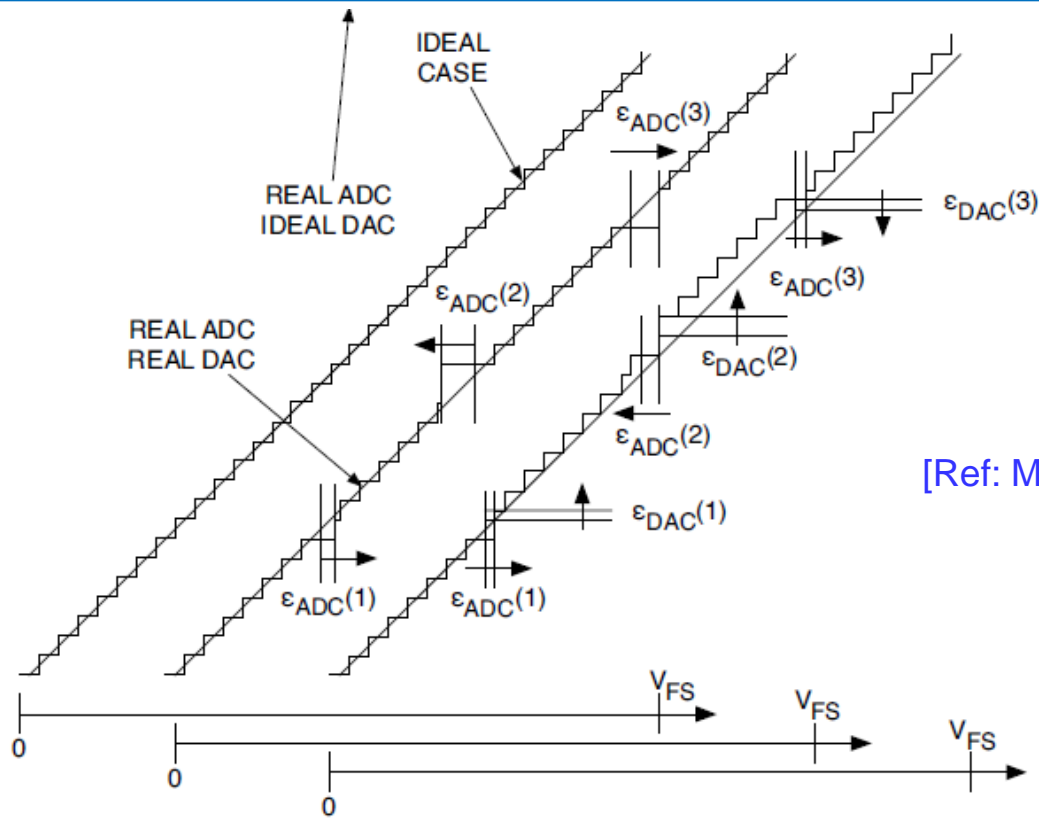


[Ref: Maloberti's book, pp. 162]

Figure 4.14. Static response of the two-step flash for ideal case and real *ADC* or *DAC*.

- Fig. 4.14 shows the input-output transfer curve for three different cases:
- ideal response (left curve), transfer characteristics with real *ADC* and ideal *DAC* (middle curve), and response with both *ADC* and *DAC* real (right curve).

Pipeline ADC (extension of 2-Step ADC)

 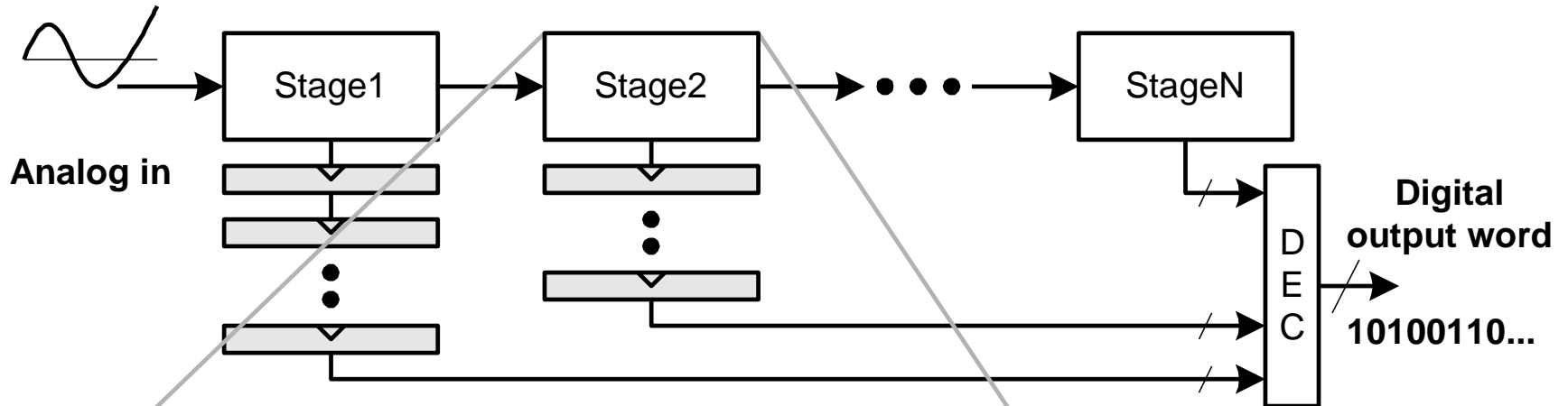

[As we will see in Next Lecture,.....]

References

- Professor Boris Murmann Course slides 2012, Stanford University- **EE315B course**
- Professor Lotfi course slides, Ferdowsi University of Mahhad.

