

EXERCISE IDEAL OP AMP ANALYSIS

No.1 Assuming ideal op amps, determine V_o for each and every circuit shown below.

